

Lab1 – Bitwise Not Circuit

By: Brandon Anderson

This circuit takes 4 inputs and outputs the opposite of the input. For example, if you input 1111 then 0000 is your output. If you input 1010, then 0101 is your output.

