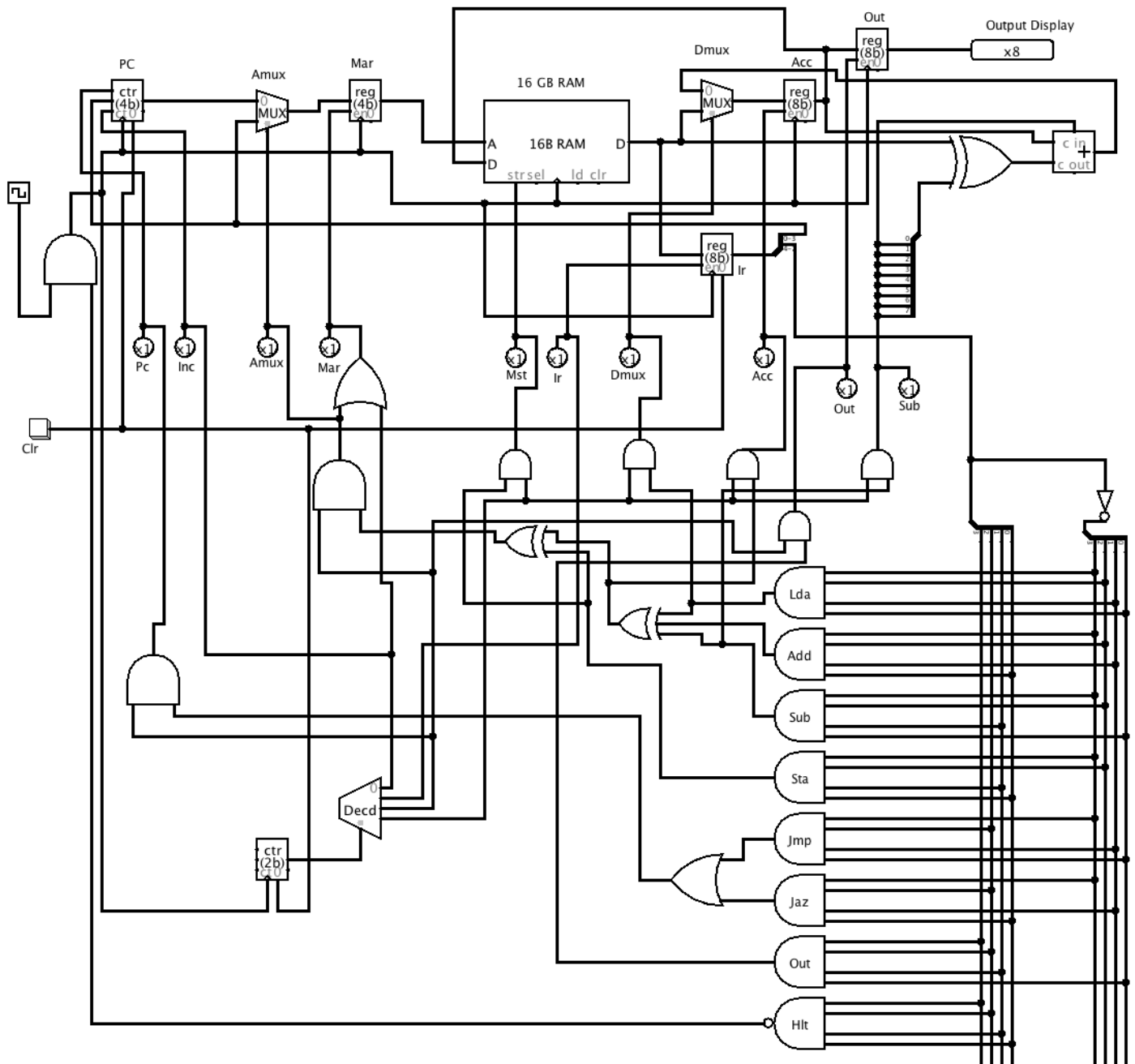


### Sam Datapath with control logic(EXCEPT JAZ= no acc check)



- a) Tested all the instructions on the datapath and they worked.
- b) Tested all the instructions on the control sequencer and they all worked except for Jaz. I have to make the logic to test if the accumulator is 0, and then implement that into the Jaz.